

Template Week 2 – Logic

Student number: 568209

Use chatCpt for better English writing

Assignment 2.1: Parking lot

Which gates do you need?

We need (AND) gate because it precisely models the condition where all parking spot are occupied (all inputs = 1), and it ensures the “FULL” sign is activated in this case.

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Assignment 2.2: Android/iPhone

Which gates do you need?

XOR gate, the XOR gate outputs 1 when exactly one input is 1, and outputs 0 if both inputs are 0 or both are 1, this models this condition when the employee can pick only one phone.

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	0

Assignment 2.3: Four NAND gates

Complete this table

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

How can the design be simplified?

1.The first NAND gate receives A,A which produces: $\text{NAND}(A,A) = \neg A$

So its output is $\neg A$ (NOT A)

2. similarly , the second NAND gate receives B , B producing : $\text{NAND} (B,B) = \neg B$

So its output is $\neg B$ (not B)


3. the third NAND gate receives the outputs $\neg A, \neg B$, producing: $\text{NAND} (\neg A , \neg B) = \neg(\neg A , \neg B)$

4. the fourth NAND gate combines the output $\neg A \neg B$ and the input from an earlier stage to produces Q.

Simplifying, we find that Q is equivalent to $A.B$, as the logic design mimics an AND gate.


Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:

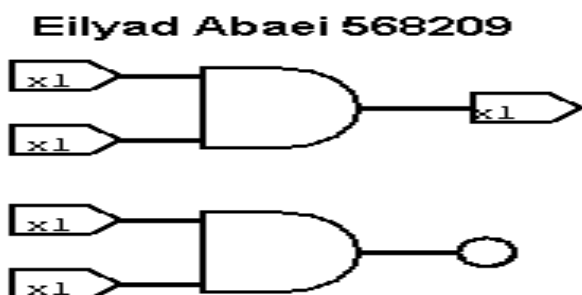


Assignment 2.5: SR Latch

Screenshot SR Latch in Logisim with your name and student number:

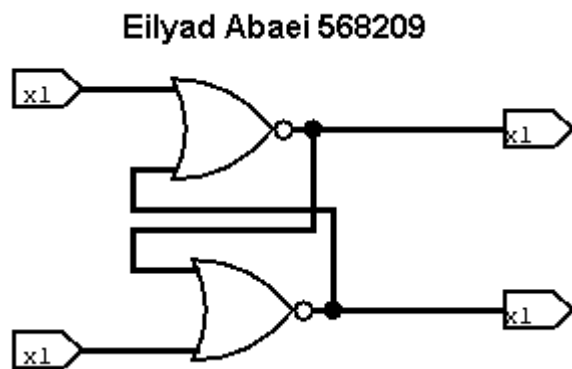

Assignment 2.6: Vending Machine

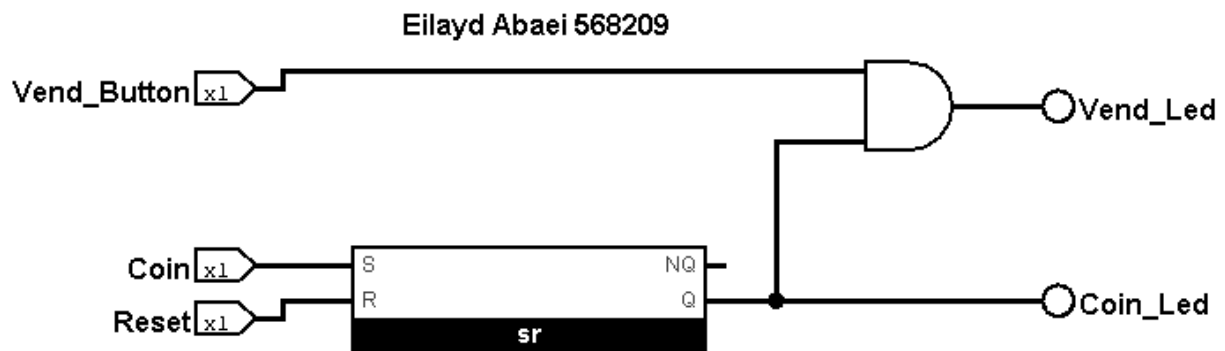Screenshot Vending Machine in Logisim with your name and student number:



Bonus point assignment – week 2

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

4. Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Paste source code here, with a screenshot of a working application

```
public class Main {  
    public static void main(String[] args) {  
        int number = 121;  
        if((number&1)==1){  
            System.out.println(" number is odd" );  
        }else{  
            System.out.println(" number is even" );  
        }  
    }  
}
```

number is odd

```
public class Main {  
    public static void main(String[] args) {  
        int number = 4;  
  
        if ((number & (number - 1)) == 0 && number > 0) {  
            System.out.println("power of two");  
        } else {  
            System.out.println("not power of two");  
        }  
    }  
}
```

not power of two

```
public class Main {  
    public static void main(String[] args) {  
        int number = 5;  
        int result = (~number +1);  
        System.out.println(result);  
    }  
}
```

-5